Incubator eletronics

Kenneth Lausdahl Your Company / University The Other Dude His Company / University

September 3, 2020

Abstract

Short introduction to subject of the paper \dots

1 Design

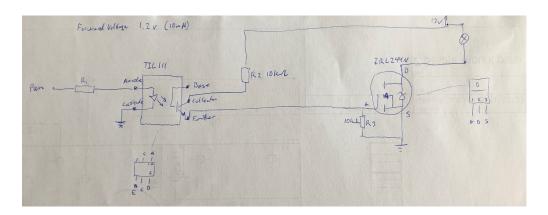


Figure 1: Overall design

1.1 Calculation of optocoupker resistor

Spec for TIL111

1. Forward Voltage 1.2v (10mA)

$$R = \frac{V}{I}$$

$$R_1 = \frac{3.3v - 1.2v}{0.010A} = 210\Omega$$
(1)

This means that the input resistor between the PI pin and the anote of the optocoupler must be at least 210 Ω so 220 Ω is a good candidate

1.2 MOSFET

Spec for IRLZ44N (N-channel mostfet:

- 1. $R_{DS_{ON}} = 0.022\Omega \ V_{GS} = 10v \ I_D = 25A$
- 2. $V_{GS} = 16V$ max gate voltage
- 3. 175 °C max operation temp
- 4. $V_{CS(th)} = 1v$
- 5. $R_{BJ}A = 62 \, {}^{\circ}\text{C/W}$

Heat disipation assuming a heated bed plate with this spec is powered:

- 1. $R = 1.65\Omega$ for 12v
- 2. P = 87w
- 3. A = 7.25A

Calculate watts for when powering the heated bed

$$P = R * I^{2}$$

$$= 22mA * 7.25^{2} = 1156mW = 1.156W$$
(2)

Calculate watts the MOSFET can handle withtout cooling

$$P_D = \frac{max(T_J) - T_A}{R_{\wp JA}}$$

$$= \frac{175^{\circ}C - 25^{\circ}C}{62} = 2.4W$$
(3)

So to use it without a heat sink we need 1.156W < 2.4W which it is so no heat sink required.

Calculating resistors between the optocoupker and mosfet. Two resistors are required. One to pull down the gate when not powered here a $10K\Omega$ or similar is fine the smaller the faster it turns off. The other resistor is required to make a voltage devider to protect the gate input voltage of the MOSFET which has a max input voltage of $V_{GS}=16v$. This means if we power it by 12v then nothing is needed but for other reasons a resistor should be added, bla bla.. So we chose to design it to also allow for 24v and get both handled by the same design.

A Voltage desiver is defined as

$$V_{out} = \frac{V_s * R_2}{R_1 + R_2} \tag{4}$$

So lets find a resistor

$$V_{out} = \frac{12v * 10K\Omega}{10K\Omega + 10K\Omega} = 6v$$

$$= \frac{24v * 10K\Omega}{10K\Omega + 10K\Omega} = 12v$$
(5)

So we see that both of these gives a voltage less than V_{gs} i.e. 12v < 16v so this resistor value is fine. The value is also above $V_{CS(th)}$ so it is enough to turn it on

1.3 A first version of the schematics

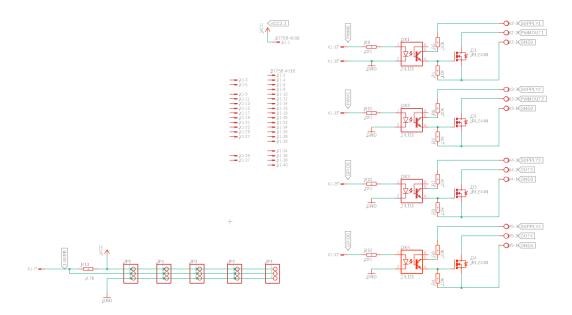


Figure 2: Schematics